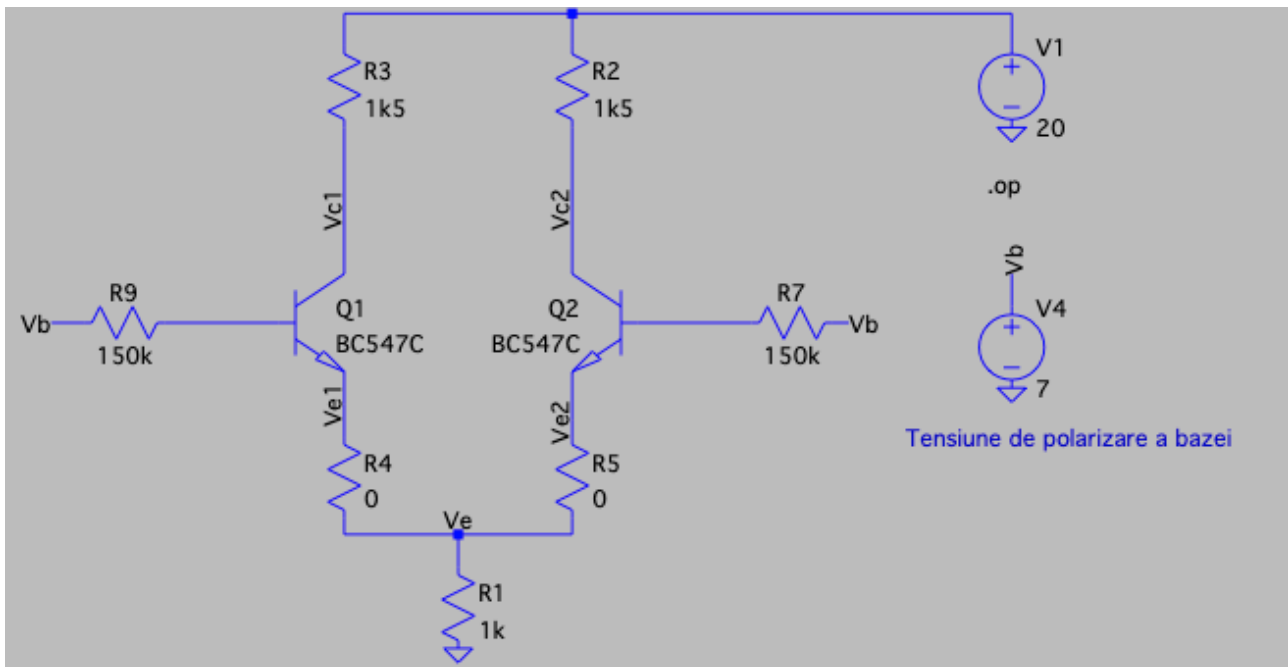


## Activitate practică Laborator 4

### 3.1 Importanta circuitului de polarizare

1.




```
Operating Bias Point Solution:
V(vc1)      15.8308    voltage
V(n002)      6.21433   voltage
V(ve)        5.56943   voltage
V(vc2)      15.8308    voltage
V(n003)      6.21433   voltage
V(n001)      20         voltage
V(vb)        7          voltage
Ic(Q2)       0.00277948 device_current
Ib(Q2)       5.23781e-06 device_current
Ie(Q2)       -0.00278472 device_current
Ic(Q1)       0.00277948 device_current
Ib(Q1)       5.23781e-06 device_current
Ie(Q1)       -0.00278472 device_current
I(R1)        0.00556943 device_current
I(R9)       -5.23781e-06 device_current
I(R7)        5.23781e-06 device_current
I(R3)        0.00277948 device_current
I(R2)        0.00277948 device_current
I(V4)       -1.04756e-05 device_current
I(V1)       -0.00555896 device_current
```

$$U_{ce} = V_{c1} - V_{ve} \Rightarrow U_{ce} = 15.8308 - 5.56943$$

$$U_{ce} = 10.26137 \text{ V}$$

$$I_c = 0.00277948 \text{ A} \Rightarrow I_c = 2.77948 \text{ mA}$$

2.

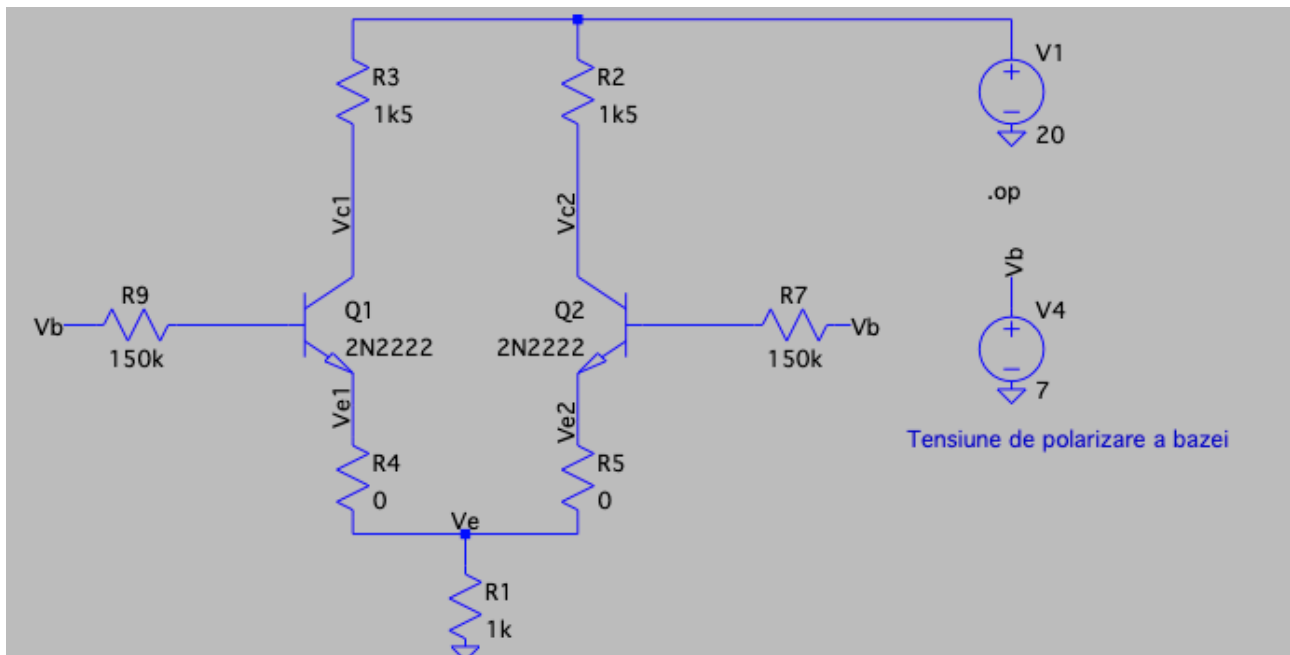

```

Operating Bias Point Solution:
V(vc1)          16.472   voltage
V(n002)          5.40061 voltage
V(ve)           4.72533   voltage
V(vc2)          16.472   voltage
V(n003)          5.40061 voltage
V(n001)          20      voltage
V(vb)            7       voltage
Ic(Q2)           0.002352 device_current
Ib(Q2)           1.06626e-05 device_current
Ie(Q2)           -0.00236266 device_current
Ic(Q1)           0.002352 device_current
Ib(Q1)           1.06626e-05 device_current
Ie(Q1)           -0.00236266 device_current
I(R1)            0.00472533 device_current
I(R9)            -1.06626e-05 device_current
I(R7)            1.06626e-05 device_current
I(R3)            0.002352 device_current
I(R2)            0.002352 device_current
I(V4)            -2.13251e-05 device_current
I(V1)            -0.004704 device_current
  
```


$$U_{ce} = V_{c1} - V_{ve} \Rightarrow U_{ce} = 16.472 - 4.72533$$

$$U_{ce} = 11.74667 \text{ V}$$

$$I_c = 0.002352 \text{ A} \Rightarrow I_c = 2.352 \text{ mA}$$

In cele doua cazuri de mai sus obtinem valori diferite ale punctelor statice de functionare ale tranzistoarelor. => Este prezenta o dependenta **clara** intre punctele statice de functionare calculate si masurate anterior si modelul tranzistoarelor utilizate.

3.

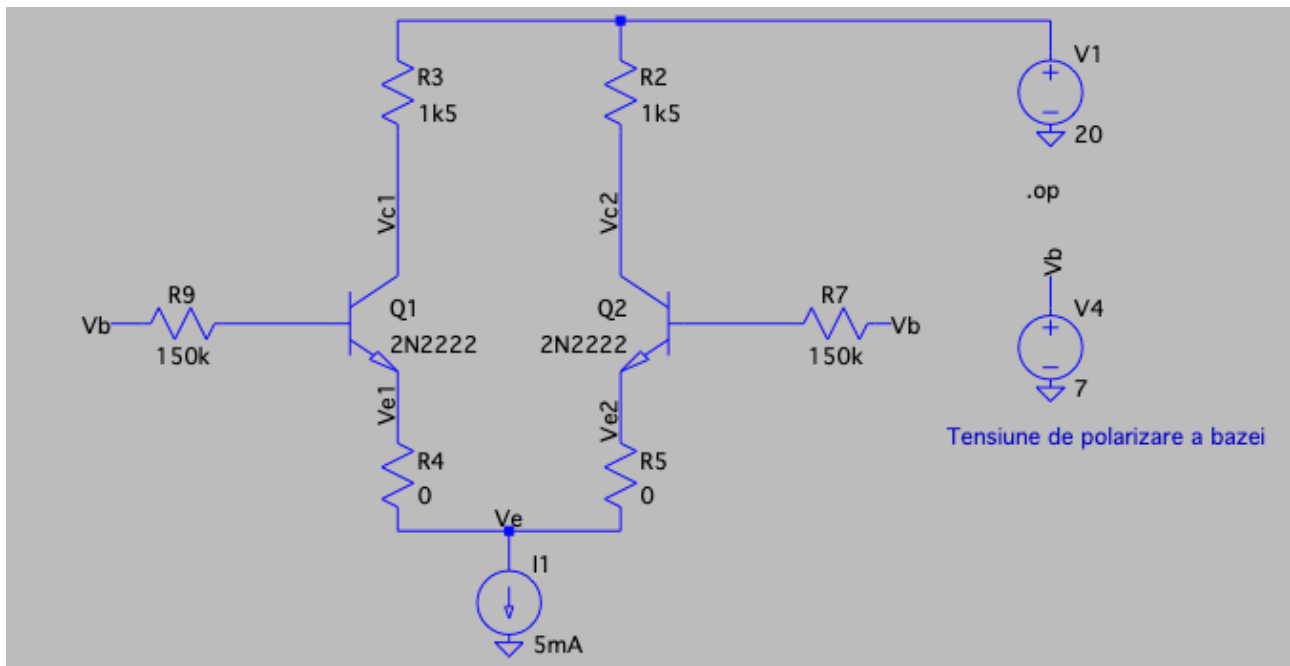

```


Operating Bias Point Solution:
V(vc1)          16.2669    voltage
V(n002)          5.30528   voltage
V(ve)           4.62846    voltage
V(vc2)          16.2669    voltage
V(n003)          5.30528   voltage
V(n001)          20        voltage
V(vb)            7         voltage
Ic(Q2)           0.0024887  device_current
Ib(Q2)           1.12981e-05 device_current
Ie(Q2)           -0.0025    device_current
Ic(Q1)           0.0024887  device_current
Ib(Q1)           1.12981e-05 device_current
Ie(Q1)           -0.0025    device_current
I(I1)            0.005      device_current
I(R9)            -1.12981e-05 device_current
I(R7)            1.12981e-05 device_current
I(R3)            0.0024887  device_current
I(R2)            0.0024887  device_current
I(V4)            -2.25963e-05 device_current
I(V1)            -0.0049774 device_current
  
```

$$U_{ce} = V_{c1} - V_{ve} \Rightarrow U_{ce} = 16.2669 - 4.62846$$

$$U_{ce} = 11.63844 \text{ V}$$

$$I_c = 0.0024887 \text{ A} \Rightarrow I_c = 2.4887 \text{ mA}$$

4.

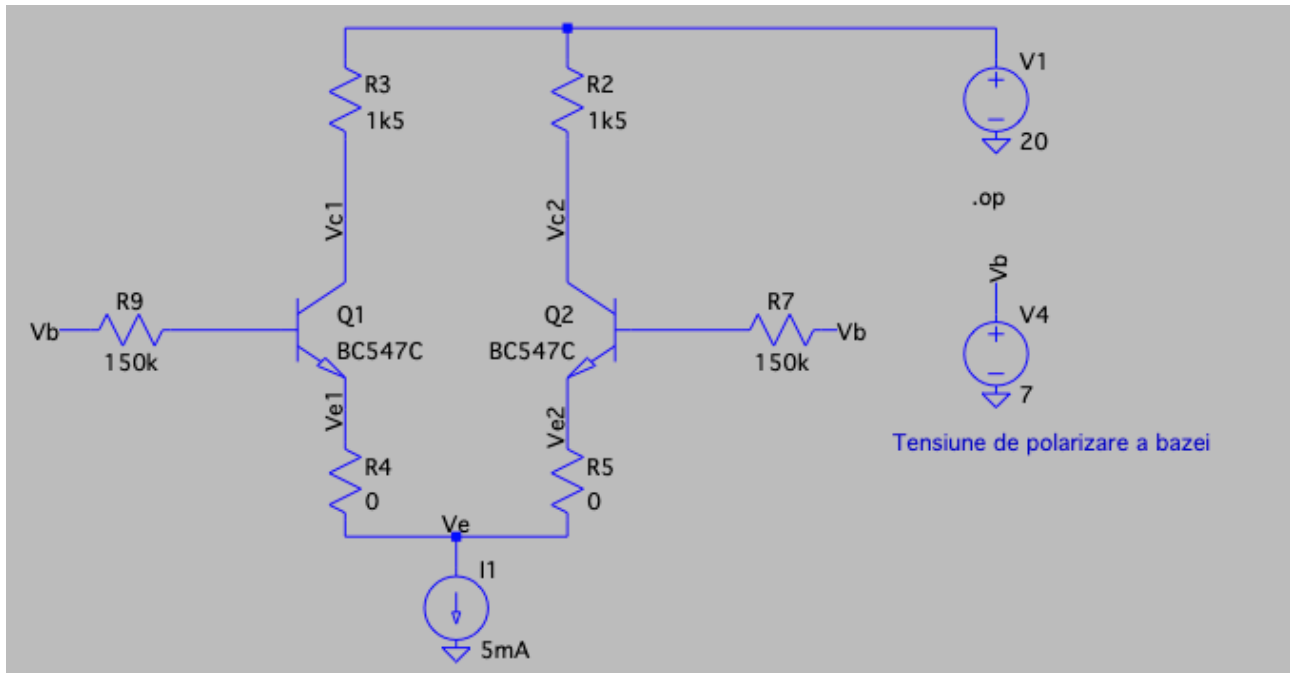

```

Operating Bias Point Solution:
V(vc1)          16.257    voltage
V(n002)         6.29967   voltage
V(ve)           5.65786   voltage
V(vc2)          16.257    voltage
V(n003)         6.29967   voltage
V(n001)         20        voltage
V(vb)           7         voltage
Ic(Q2)          0.00249533 device_current
Ib(Q2)          4.66888e-06 device_current
Ie(Q2)          -0.0025    device_current
Ic(Q1)          0.00249533 device_current
Ib(Q1)          4.66888e-06 device_current
Ie(Q1)          -0.0025    device_current
I(I1)           0.005      device_current
I(R9)           -4.66888e-06 device_current
I(R7)           4.66888e-06 device_current
I(R3)           0.00249533 device_current
I(R2)           0.00249533 device_current
I(V4)           -9.33776e-06 device_current
I(V1)           -0.00499066 device_current
  
```

$$U_{ce} = V_{c1} - V_{ve} \Rightarrow U_{ce} = 16.257 - 5.65786$$


$$U_{ce} = 10.59914 \text{ V}$$

$$I_c = 0.00249533 \text{ A} \Rightarrow I_c = 2.49533 \text{ mA}$$

Valorile punctelor statice de functionare ale tranzistoarelor difera fata de cazurile de mai sus. Intensitatea este aproape neschimbata. Imbunatatirea adusa de utilizarea sursei de curent in locul rezistentei de cuplaj este faptul ca se forteaza o scurgere de 5mA catre sursa.

### 3.2 Determinarea amplificarii diferentiale

1.

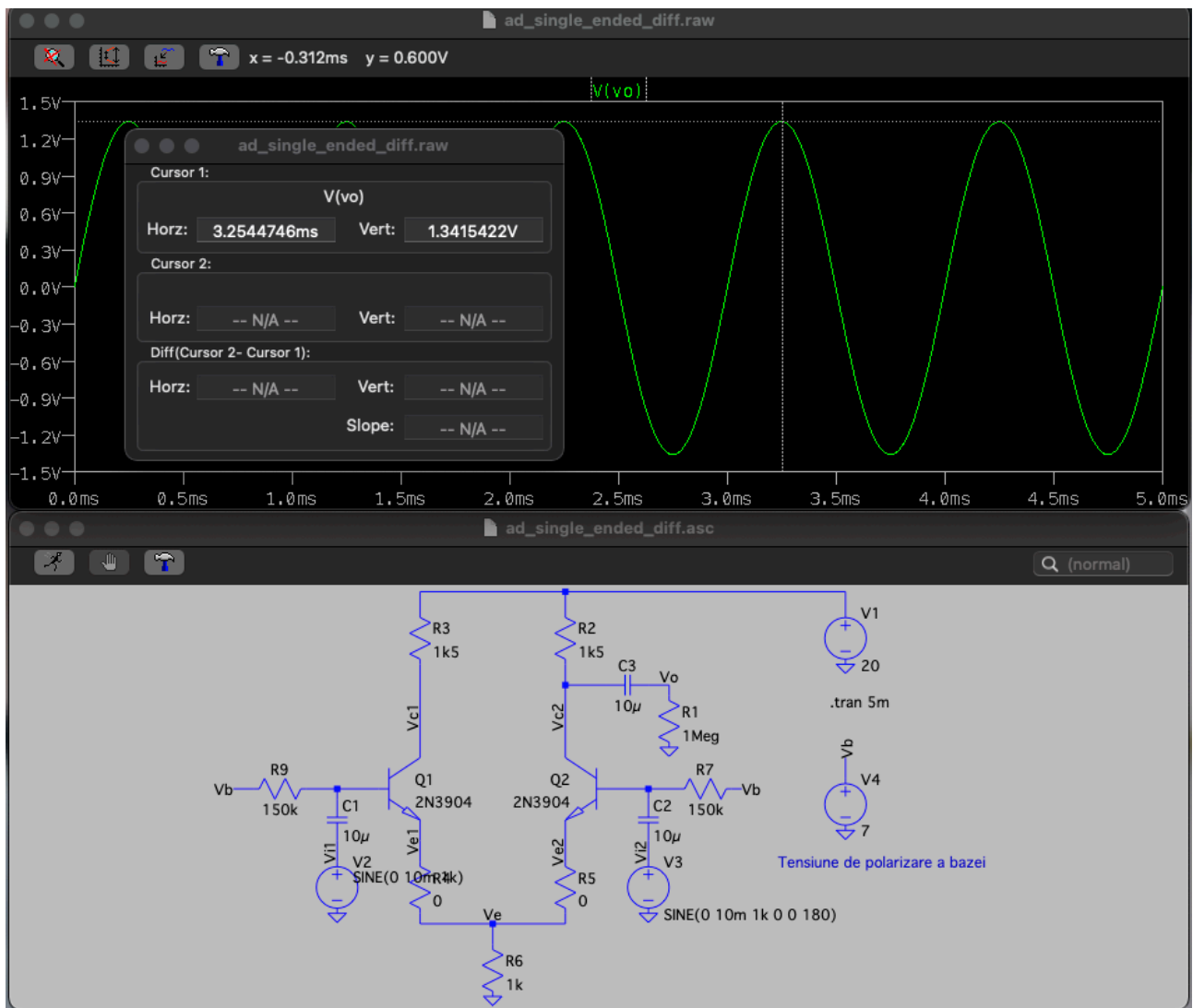

$$V_0 = 1.341 \text{ V}$$


$$A_d = V_0 / (V_2 - V_3)$$

$$V_2 = 10 \text{ mV}$$

$$V_3 = -10 \text{ mV (defazaj 180 grade)}$$

$$\Rightarrow A_d = 1.341 / (10 - (-10)) = 67.05$$

2.

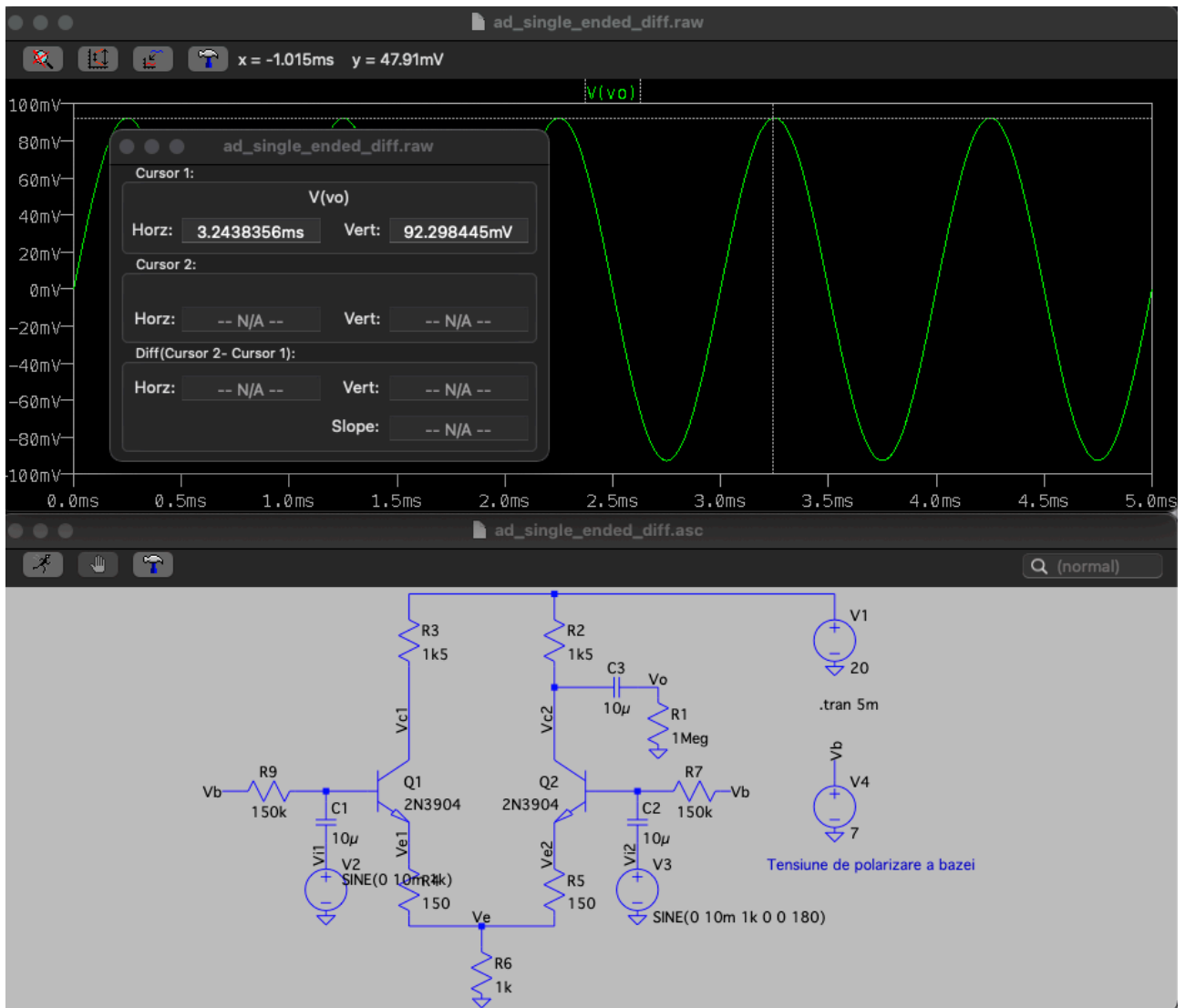

$$V_0 = 92.298 \text{ mV}$$

$$A_d = V_0 / (V_2 - V_3)$$

$$V_2 = 10 \text{ mV}$$


$$V_3 = -10 \text{ mV (defazaj 180 grade)}$$

$$\Rightarrow A_d = 92.298 / (10 - (-10)) = 4.6149$$

In acest caz amplificarea diferentiala este mai mica deoarece  $V_0$  este mai mica.

### 3.3 Determinarea amplificarii de mod comun. Influenta rezistentei de cuplaj a emitoarelor asupra factorului de rejectie a modului comun.


1.

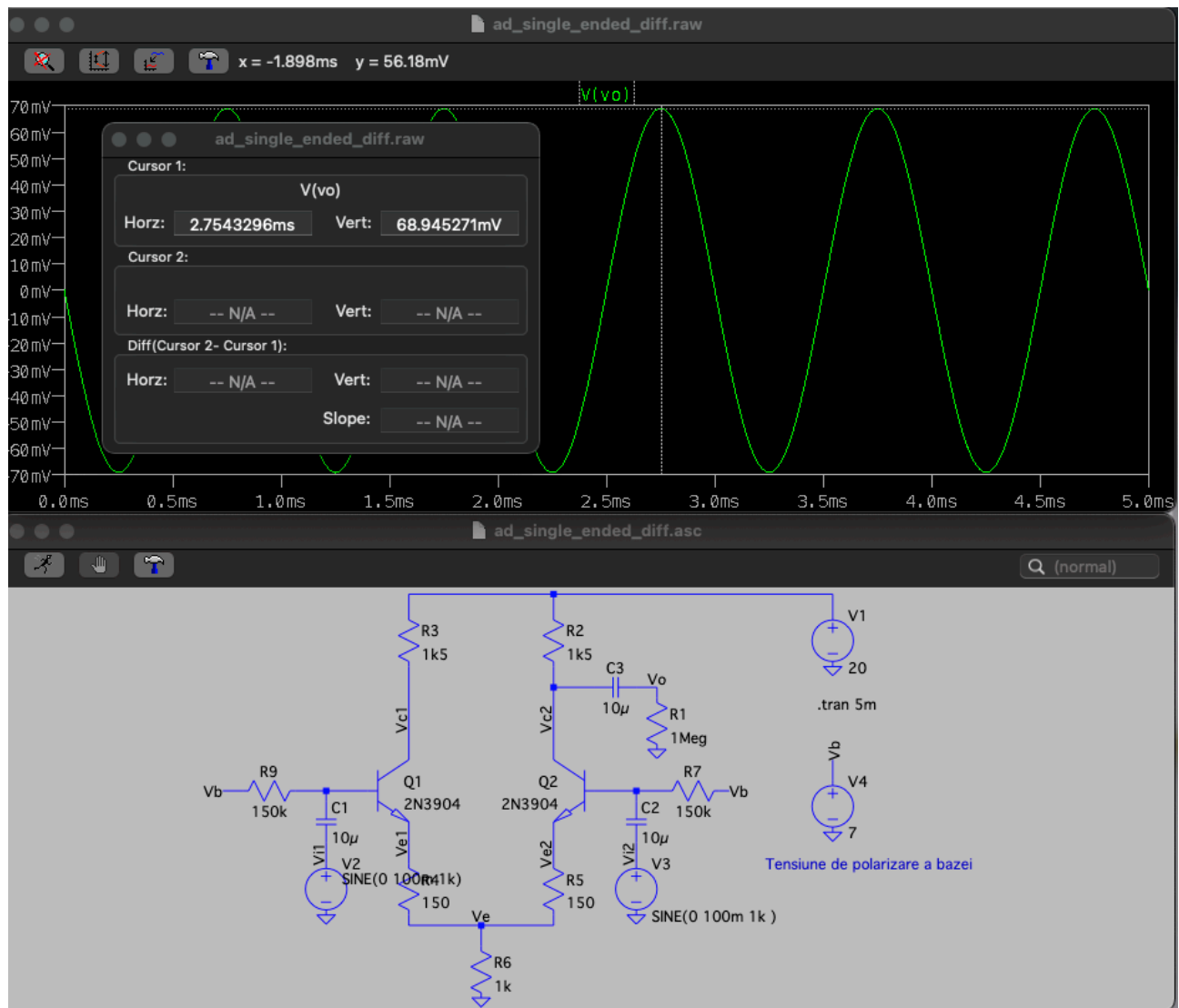

$$V0 = 68.945 \text{ mV}$$

$$V0 = A_d (V_{i1} - V_{i2}) + A_c ((V_{i1} + V_{i2}) / 2) \Rightarrow V0 = A_c V_{i1} \Rightarrow A_c = V0 / V1$$
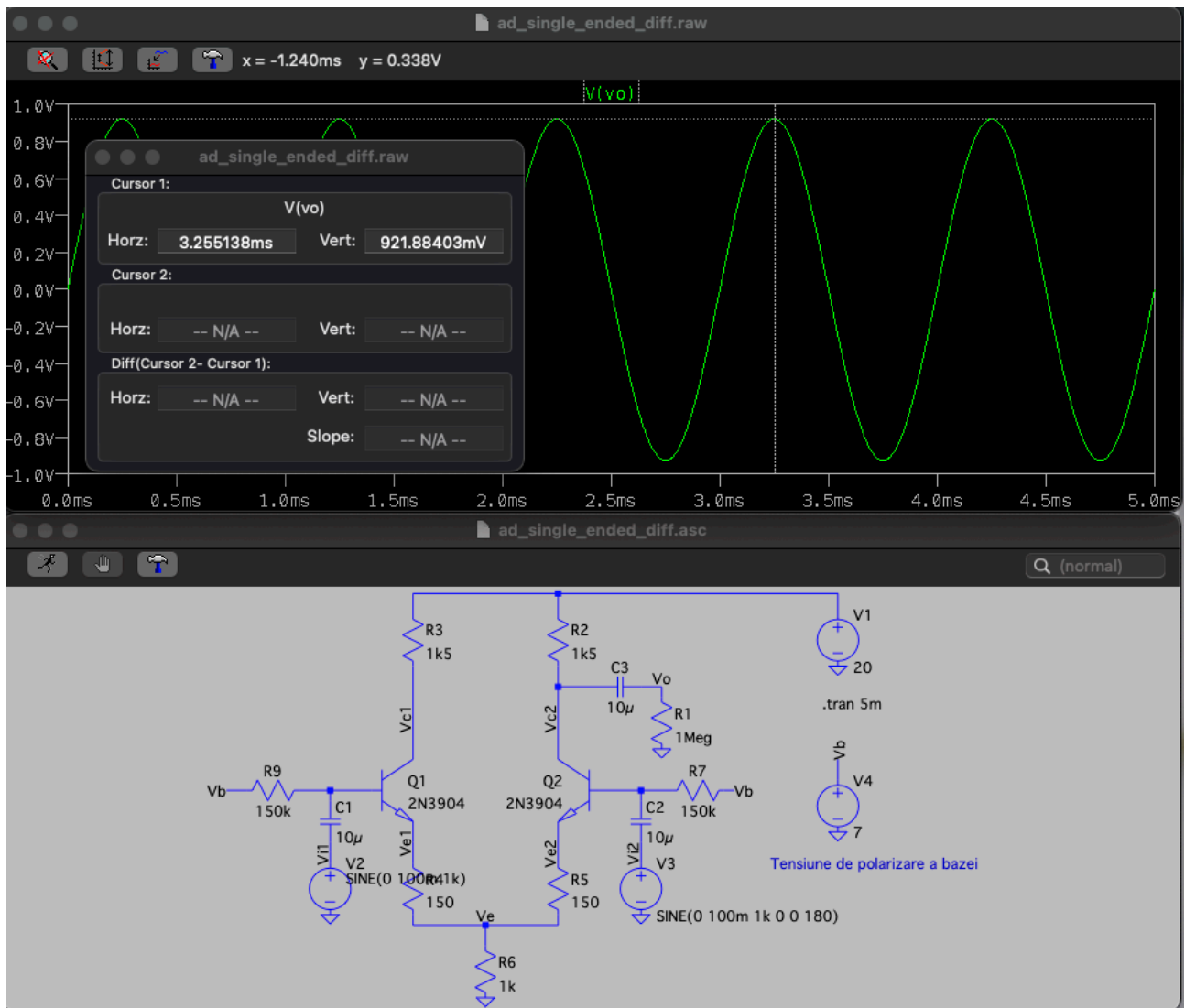
$$A_c = V0 / V_{i1} \Rightarrow A_c = 68.945 / 100 = 0.68945 \text{ mV (amplificare in mod comun)}$$



$$V_0 = 921.884 \text{ mV}$$


$$A_d = V_0 / (V_{i1} - V_{i2}) \Rightarrow A_d = 921.884 / (100 - (-100)) = 4.60942 \text{ mV}$$

$$\text{CMRR} = 20 \log_{10} (A_d / A_c) \Rightarrow \text{CMRR} = 20 \log_{10}(4.60942 / 0.68945)$$

$$\text{CMRR} = 16.5028701186 \text{ dB}$$



2.

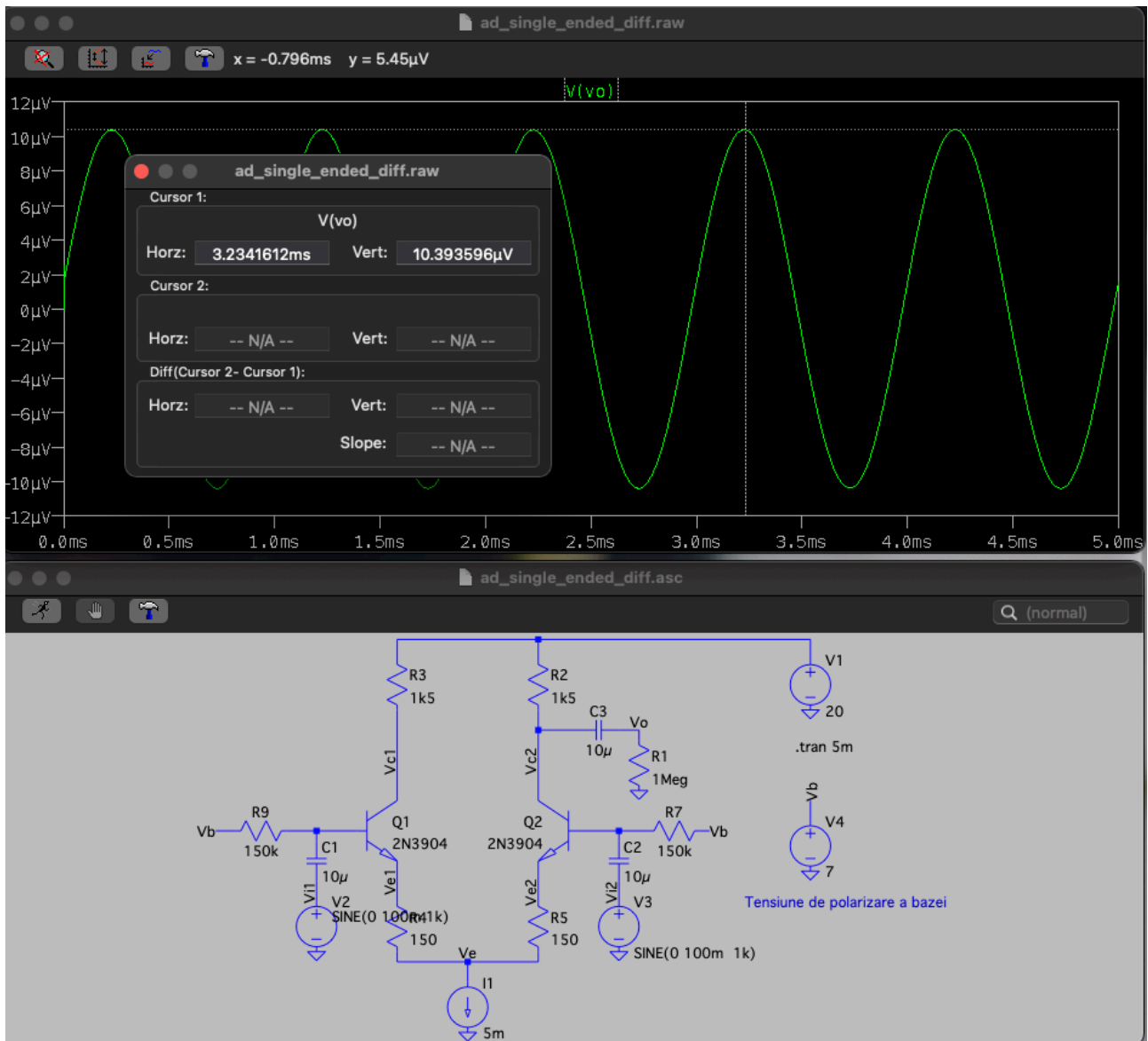


$$V_0 = 10.393 \mu V$$

$$V_0 = A_d (V_{i1} - V_{i2}) + A_c ((V_{i1} + V_{i2}) / 2) \Rightarrow V_0 = A_c V_{i1} \Rightarrow A_c = V_0 / V_1$$

$$A_c = V_0 / V_{i1} \Rightarrow A_c = 10.393 / 100 = 10.393 * 100000 mV$$

(amplificare in mod comun)

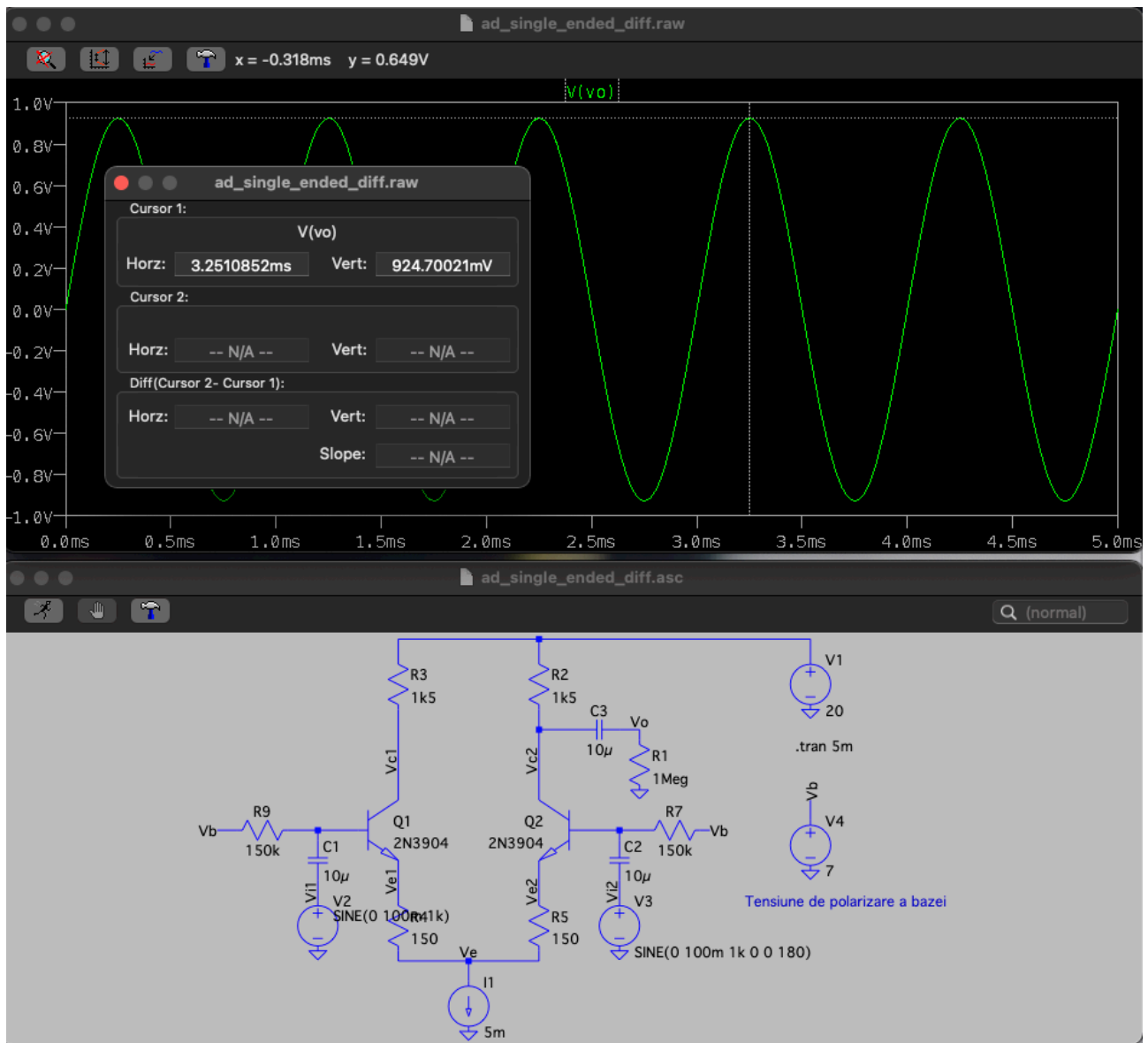

$$V_0 = 924.700 \text{ mV}$$

$$A_d = V_0 / (V_{i1} - V_{i2}) \Rightarrow A_d = 924.700 / (100 - (-100)) = 4.6235 \text{ mV}$$

$$\text{CMRR} = 20 \log_{10} (A_d / A_c) \Rightarrow \text{CMRR} = 20 \log_{10}(4.6235 / 10.393 * 100000)$$

$$\text{CMRR} = 92.9645986936 \text{ dB}$$

Noua valoare a factorului de rejectie a modului comun este mai mare in cazul actual fata de cel de la 3.1, fapt din care rezulta ca avem o rejectie eficienta.

CMRR se maresc odata cu rezistenta de cuplaj a tranzistoarelor.